

Digital Logic Design

Lecture 06: Combinational Logic Circuit & Boolean Algebra

What is Boolean Algebra

- An algebra dealing with
 - Binary variables by alphabetical letters
 - Logic operations: OR, AND, XOR, etc
- Consider the following Boolean equation

$$F(X,Y,Z) = \overline{X \cdot Y} + \overline{Y \cdot Z} + Z$$

- A Boolean function can be represented by a truth table which list all combinations of 1's and 0's for each binary value

Fundamental Operators

- NOT
 - Unary operator
 - Complements a Boolean variable represented as A' , $\sim A$, or \bar{A}
- OR
 - Binary operator
 - A ORed with B is represented as $A + B$
- AND
 - Binary operator
 - A ANDed with B is represented as AB or $A \cdot B$
 - Can perform logical multiplication

Precedence of Operators

- Precedence of Operator Evaluation (Similar to decimal arithmetic)

- () : Parentheses
- NOT
- AND
- OR

$$F = A \cdot \overline{(B + \overline{C \cdot D})} + \overline{A} \cdot \overline{B} + E$$

Function Evaluation

$$F = A \cdot \overline{(B + \overline{C \cdot D})} + \overline{A} \cdot \overline{B} + E$$


ABCDE=00000

$$\begin{aligned} F &= 0 \cdot \overline{(0 + \overline{0 \cdot 0})} + \overline{0} \cdot \overline{0} + 0 = 0 \cdot \overline{(0 + 1 \cdot 0)} + 0 \cdot 1 + 0 \\ &= 0 \cdot \overline{(0 + 0)} + 1 \cdot 1 = 0 \cdot 1 + 1 \cdot 0 = 0 \end{aligned}$$

ABCDE=10000

$$\begin{aligned} F &= 1 \cdot \overline{(0 + \overline{0 \cdot 0})} + \overline{1} \cdot \overline{0} + 0 = 1 \cdot \overline{(0 + 1 \cdot 0)} + 0 \cdot 1 + 0 \\ &= 1 \cdot \overline{(0 + 0)} + 0 \cdot 1 = 1 \cdot 1 + 0 \cdot 0 = 1 \end{aligned}$$

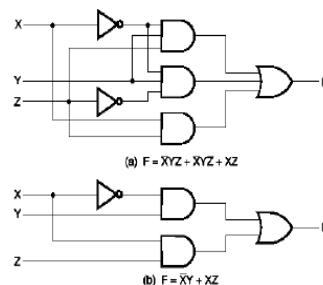Implementation of Boolean Function with Gates



Boolean Variables

- A multi-dimensional space spanned by a set of n Boolean variables is denoted by \mathcal{B}^n
- A literal is an instance (e.g. A) of a variable or its complement (\bar{A})

Basic Identities of Boolean Algebra

$X + 0 = X$	(Identity)
$X + 1 = 1$	
$X + \bar{X} = 1$	(Complement)
$\bar{\bar{X}} = X$	(Involution Law)
$X + Y = Y + X$	(Commutative)
$X + (Y + Z) = (X + Y) + Z$	(Associative)
$X(Y + Z) = XY + XZ$	(Distributive)
$\overline{X + Y} = \bar{X}\bar{Y}$	(DeMorgan's Law)
$X + X\bar{Y} = X$	(Absorption Law)
$X + \bar{X}Y = X + Y$	(Simplification)
$XY + \bar{X}Z + YZ = XY + \bar{X}Z$	(Consensus Theorem)

Derivation of Simplification

$$\begin{aligned}
 & X + \bar{X}Y \\
 &= X \cdot (1 + Y) + \bar{X}Y \\
 &= X + XY + \bar{X}Y \\
 &= X + (X + \bar{X})Y \\
 &= X + Y \\
 &\therefore X + \bar{X}Y = X + Y
 \end{aligned}$$

Derivation of Consensus Theorem

$$\begin{aligned}
 & XY + \bar{X}Z + YZ \\
 &= XY + \bar{X}Z + YZ \cdot (X + \bar{X}) \\
 &= XY + \bar{X}Z + XYZ + \bar{X}YZ \\
 &= XY(1 + Z) + \bar{X}Z(1 + Y) \\
 &= XY + \bar{X}Z \\
 &\therefore XY + \bar{X}Z + YZ = XY + \bar{X}Z
 \end{aligned}$$

Duality Principle


- A Boolean equation remains valid if we take the dual of the expressions on both sides of the equals sign
- Dual of expressions
 - Interchange 1's and 0's
 - Interchange AND (\bullet) and OR ($+$)

Duality Principle

$X + 0 = X$	$X \cdot 1 = X$
$X + 1 = 1$	$X \cdot 0 = 0$
$X + \bar{X} = 1$	$X \cdot \bar{X} = 0$
$X + Y = Y + X$	$X \cdot Y = Y \cdot X$
$X(Y + Z) = XY + XZ$	$X + Y \cdot Z = (X + Y) \cdot (X + Z)$
$\overline{X + Y} = \bar{X} \cdot \bar{Y}$	$\overline{X \cdot Y} = \bar{X} + \bar{Y}$
$X + X \cdot Y = X$	$X \cdot (X + Y) = X$
$X + \bar{X} \cdot Y = X + Y$	$X \cdot (\bar{X} + Y) = \bar{X} \cdot Y$
$XY + \bar{X}Z + YZ = XY + \bar{X}Z$	$(X + Y)(\bar{X} + Z)(Y + Z) = (X + Y)(\bar{X} + Z)$

DeMorgan's Law
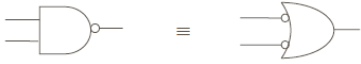
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

