

Digital Logic Design


Lecture 07: Combinational Logic Circuit & Boolean Algebra

Generalized De Morgan's Theorem


- NOT all variables
- Change $.$ to $+$ and $+$ to $.$
- NOT the result

- $F = X . Y + X . Z + Y . Z$
- $F = !((!X + !Y) . (!X + !Z) . (!Y + !Z))$
- $F = !(!(X . Y) . !(X . Z) . !(Y . Z))$

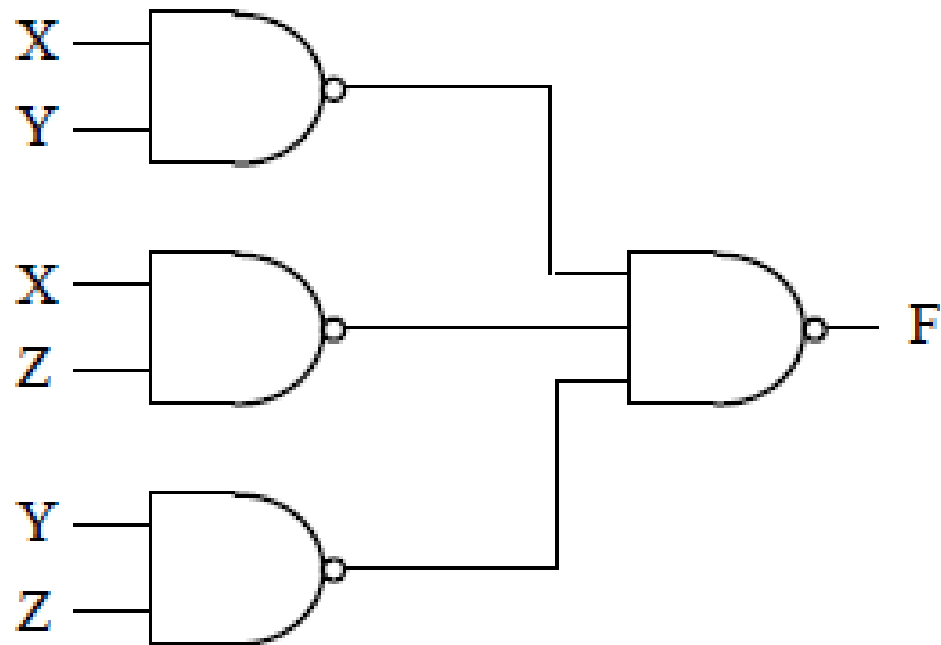
$$F = !(X \& Y) \& !(X \& Z) \& !(Y \& Z)$$


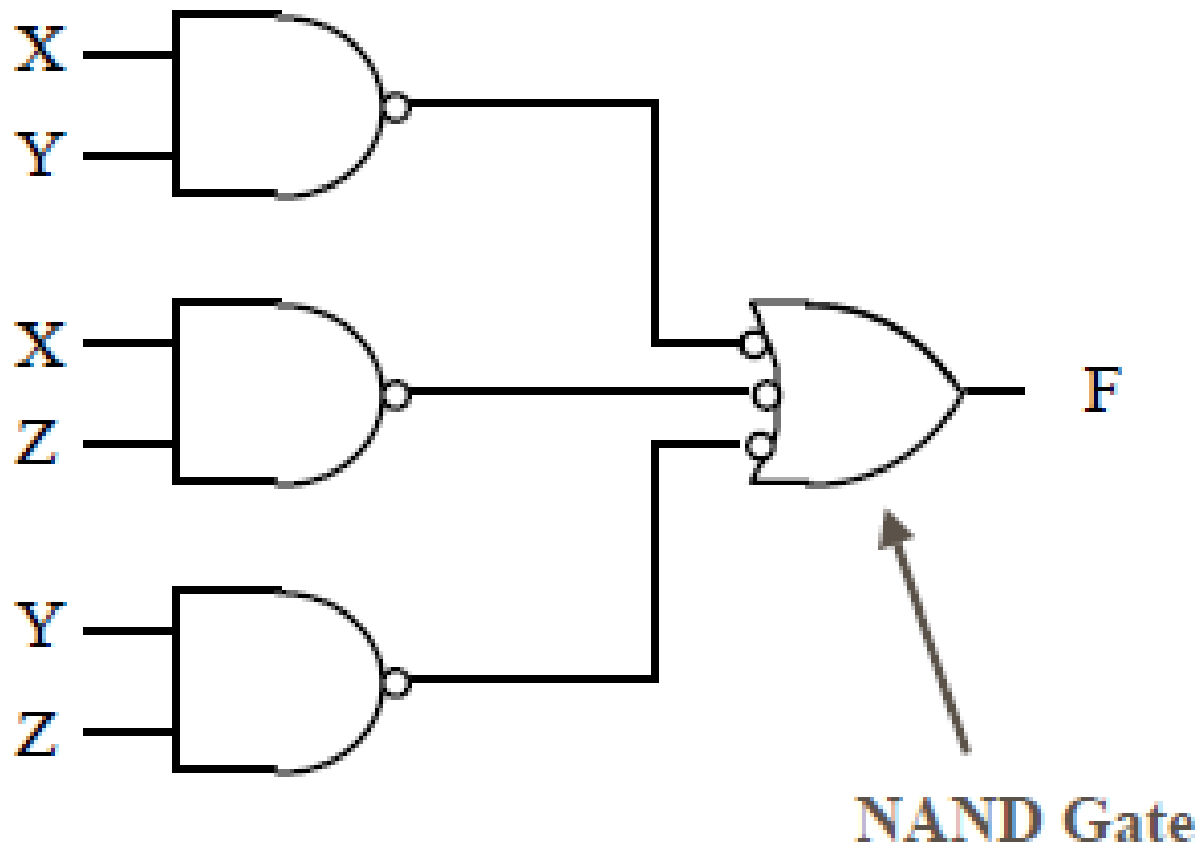
$$F = !(X \& Y) \& !(X \& Z) \& !(Y \& Z)$$



$$F = X \& Y \mid X \& Z \mid Y \& Z$$

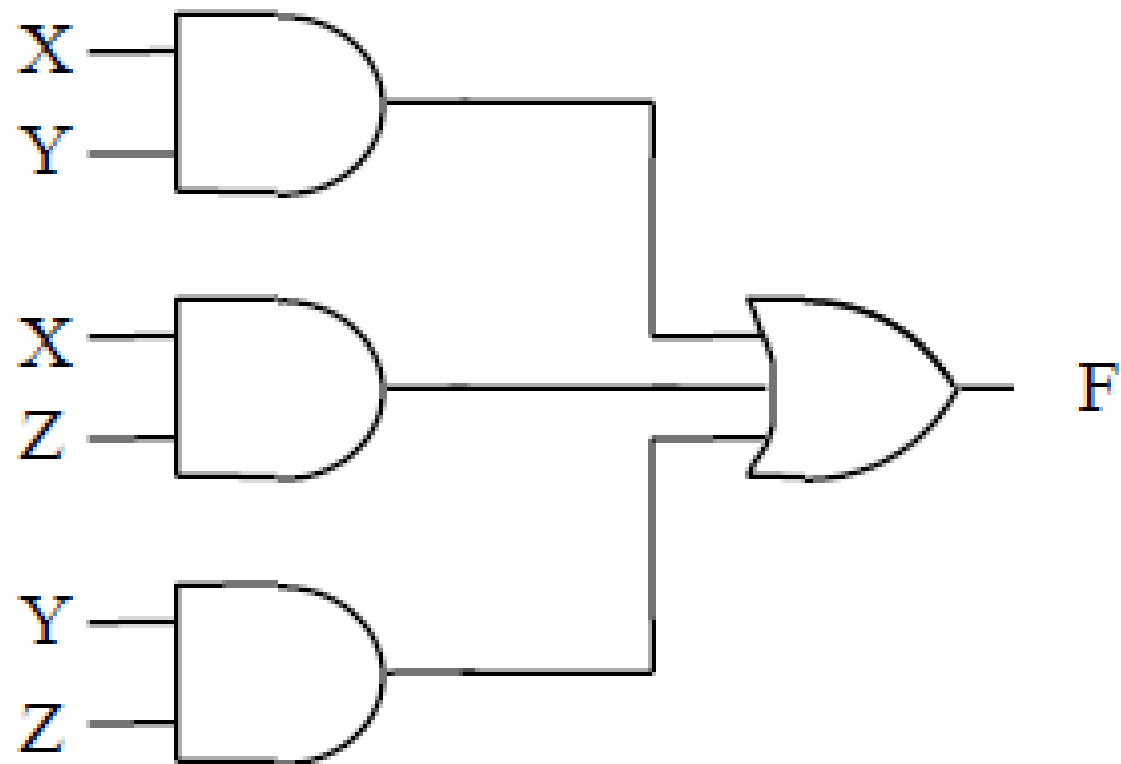

Boolean Algebra (cont)

- Sum of Products and Product of Sums
- The Duality Principal: *Interchange AND with OR*
- Algebraic Manipulations
 - $X + XY = X(1 + Y) = X$
 - $XY + XY' = X(Y + Y') = X$
 - $X + X'Y = (X + X')(X + Y) = X + Y$
 - $XY + X'Z + YZ = XY + X'Z$ -Consensus Theorem
- Complement of a Function: *Interchange all 0's with 1's in the truth table*

SOP Form

- A product of literals is called a product term or a cube (e.g. $\bar{A} \cdot B \cdot C$ in \mathcal{B}^3 , or $B \cdot C$ in \mathcal{B}^3)
- Sum-Of-Product (SOP) Form: OR of product terms, e.g. $\bar{A}B + AC$
- A minterm is a product term in which every literal (or variable) appears in \mathcal{B}^n
 - $\bar{A}BC$ is a minterm in \mathcal{B}^3 but not in \mathcal{B}^4 . $ABCD$ is a minterm in \mathcal{B}^4 .
- A canonical (or standard) SOP function:
 - a sum of minterms corresponding to the input combination of the truth table for which the function produces a "1" output.

Minterms in \mathcal{B}^3

			m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
A	B	C	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}B\bar{C}$	$\bar{A}BC$	$A\bar{B}\bar{C}$	$A\bar{B}C$	$AB\bar{C}$	ABC
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Canonical (Standard) SOP Function

$$\begin{aligned}F(A,B,C) &= \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} + \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} + \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} + \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} \\&= m_0 + m_1 + m_4 + m_5\end{aligned}$$

$$F(A,B,C) = \sum m(0,1,4,5) = \text{one-set}(0,1,4,5)$$

$$\begin{aligned}F(A,B,C,D) &= \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}}\overline{\overline{D}} + \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}}\overline{\overline{D}} + \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}}\overline{\overline{D}} \\&= m_4 + m_9 + m_{14}\end{aligned}$$

$$F(A,B,C,D) = \sum m(4,9,14) = \text{one-set}(4,9,14)$$

Product of Sums Design

Maxterms:

A maxterm is NOT a minterm

maxterm M_0 = NOT minterm m_0

$$\begin{aligned} M_0 &= \neg m_0 \\ &= \neg (\neg X \cdot \neg Y) \\ &= \neg \neg X + \neg \neg Y \\ &= X + Y \end{aligned}$$

POS form (dual of SOP form)

- A sum of literals is called a sum term (e.g. $\bar{A}+B+C$ in \mathcal{B}^3 , or $(B+C)$ in \mathcal{B}^3)
- Product-Of-Sum (POS) Form: AND of sum terms, e.g. $(\bar{A}+B)(A+C)$
- A maxterm is a sum term in which every literal (or variable) appears in \mathcal{B}^n
 - $(\bar{A}+B+C)$ is a maxterm in \mathcal{B}^3 but not in \mathcal{B}^4 .
 $A+B+C+D$ is a maxterm in \mathcal{B}^4 .
- A canonical (or standard) POS function:
 - a product of maxterms corresponding to the input combination of the truth table for which the function produces a "0" output.

Product of Sums Design

X	Y	minterms	maxterms
0	0	$m_0 = !X \cdot !Y$	$M_0 = !m_0 = X + Y$
0	1	$m_1 = !X \cdot Y$	$M_1 = !m_1 = X + !Y$
1	0	$m_2 = X \cdot !Y$	$M_2 = !m_2 = !X + Y$
1	1	$m_3 = X \cdot Y$	$M_3 = !m_3 = !X + !Y$

Maxterms in \mathcal{B}^3

[illegible]